

# Gate Question.35

Meet Patel(MIT WPU )

## Contents

### 1 PROBLEM

### 2 COMPONENTS


### 3 TRUTH TABLE

### 4 ARDUINO CONNECTIONS

### 5 CODE
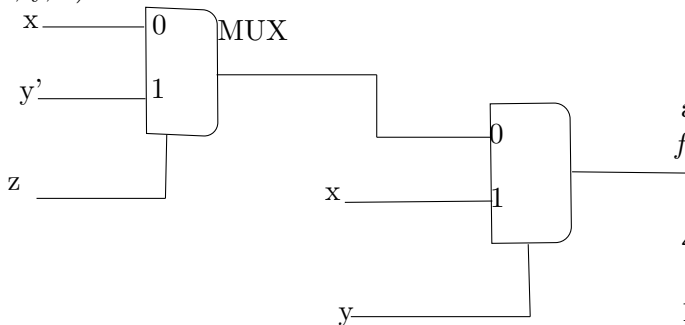
### 1 PROBLEM

(GATE CS-2006) Q.35 Consider the circuit above. Which one of the following options correctly represents  $f(x, y, z)$ ?



- (A)  $xz' + xy + y'z$   
 (B)  $xz' + xy + (yz)'$   
 (C)  $xz + xy + (yz)'$   
 (D)  $xz + xy' + y'z$

### 2 COMPONENTS

Component	Value	Quantity
Arduino	UNO	1
Bread board	-	1
Jumper wires	M-M	20
LED	-	1

### 3 TRUTH TABLE

The Truth Table for the identities got after the MUX is as follows:  $F = xz' + xy + y'z$

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Table 1

Here, Except (A) identity all other identities are valid according to the mentioned Equation .

### 4 ARDUINO CONNECTIONS

1) The connections between ARDUINO and LED are as follows:

ARDUINO	2	grnd
LED	anode	cathode

Table 2

2) The connections between Inputs( $x, y, z$ ) and Arduino are as follows:

Inputs	$x$	$y$	$z$
ARDUINO	6	7	8

Table 3

3) The inputs  $x, y, z$  here are connected to Arduino D6, D7, D8 pins.

4) The values for these inputs are connected either to GND or 5V according to the truth table.

## 5 CODE

The arduino code can be downloaded from the below link.

```
https://github.com/meet-304/meet-304/  
tree/main/src/Arduino.ino
```