

Gate Question.35

Meet Patel(MIT WPU)

Contents

1 PROBLEM

2 COMPONENTS


3 TRUTH TABLE

4 ARDUINO CONNECTIONS

5 CODE

1 PROBLEM

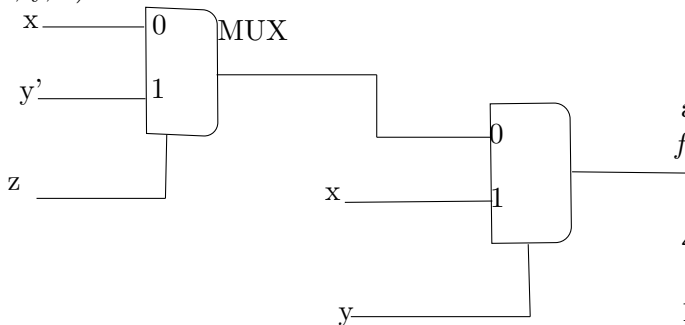(GATE CS-2006) Q.35 Consider the circuit above. Which one of the following options correctly represents $f(x, y, z)$?



- (A) $xz' + xy + y'z$
 (B) $xz' + xy + (yz)'$
 (C) $xz + xy + (yz)'$
 (D) $xz + xy' + y'z$

2 COMPONENTS

Component	Value	Quantity
Arduino	UNO	1
Bread board	-	1
Jumper wires	M-M	20
LED	-	1

3 TRUTH TABLE

The Truth Table for the above identities is as follows:

$$F = xz' + xy + y'z$$

1

1

1

2

x	y	z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Table 1

Here, Except (A) identity all other identities are valid according to the mentioned Equation .

4 ARDUINO CONNECTIONS

1) The connections between ARDUINO and LED are as follows:

ARDUINO	2	grnd
LED	anode	cathode

Table 2

2) The connections between Inputs(x,y,z) and Arduino are as follows:

Inputs	x	y	z
ARDUINO	6	7	8

Table 3

3) The inputs **x,y,z** here are connected to Arduino D6,D7,D8 pins.

4) The values for these inputs are connected either to GND or 5V according to the truth table.

5 CODE

The arduino code can be downloaded from the below link.

```
https://github.com/madhu-addanki/FWC/  
tree/main/ide
```